

# Construction of PV Module using MATLAB-SIMULINK

Power & Control Engineering Experiment  
T.A. : Cholmin Kim (Smartgrid Lab)  
Contact : calvin16@yonsei.ac.kr

## ❖ Progress Chart

		Week 1		Week 2	
Class 1	Boost Converter	[Red bar]			
	PV Connection	[Red bar]			
Class 2	Single-Phase Inverter			[Red bar]	
	PV Single-Phase Inverter			[Red bar]	

- I-V and P-V curve and operation of PV array
- Concept of Maximum Power Point Tracking (MPPT) of PV
- Duty ratio and operation of boost converter
- Concept of PWM switching control

- Learn a basic usage of MATLAB/SIMULINK simulation tool
- Learn a basic concept of boost converter switching operation and duty ratio( $D$ ) with PWM control
- Learn a basic concept of duty ratio control with Maximum Power Point Tracking (MPPT) in boost converter connected a PV array

## ❖ Semiconductor Devices


- Bipolar Junction Transistor(BJT)
  - The BJT is a type of transistor that uses both electrons and holes as charge carriers. BJT is controlled by the input base current.
- Metal-Oxide-Semiconductor Field-Effect Transistor(MOSFET)
  - MOSFET is a type of field-effect transistor(FET), most commonly fabricated by the controlled oxidation of silicon. MOSFET is controlled by the input gate voltage.
- **Insulated-Gate Bipolar Transistor(IGBT)**
  - IGBT is a three-terminal semiconductor device used as an high efficiency and fast switching.
  - The IGBT combines the simple gate-drive characteristics of MOSFETs with the high-current and low-saturation-voltage capability of BJTs.

Device Characteristic	Power Bipolar	Power MOSFET	IGBT
Voltage Rating	High <1kV	High <1kV	Very High >1kV
Current Rating	High <500A	Low <200A	High >500A
Input Drive	Current, $h_{FE}$ 20-200	Voltage, $V_{GS}$ 3-10V	Voltage, $V_{GE}$ 4-8V
Input Impedance	Low	High	High
Output Impedance	Low	Medium	Low
Switching Speed	Slow ( $\mu$ S)	Fast (nS)	Medium
Cost	Low	Medium	High


<Comparison Table>

## ❖ Photovoltaic System


### ■ Solar Cell

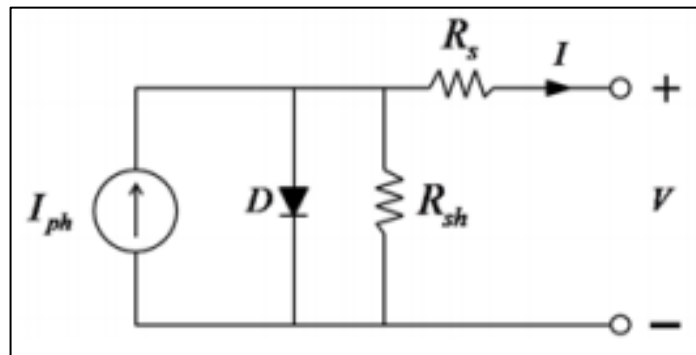


< PV Cell circuit model >

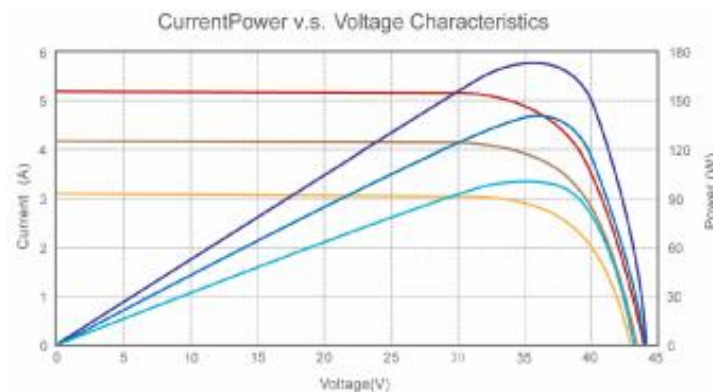

<PV I-V & P-V Curve>

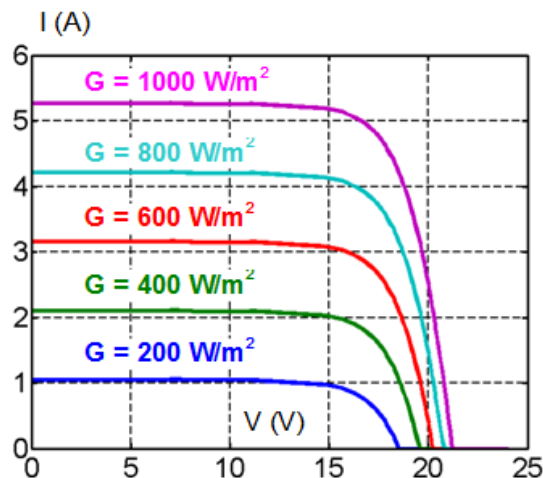


< PV Power vs Irradiance >

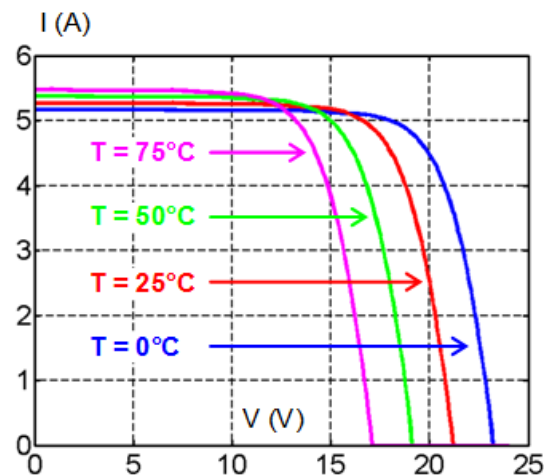


< PV Power vs Temperature >

## ❖ PV Array

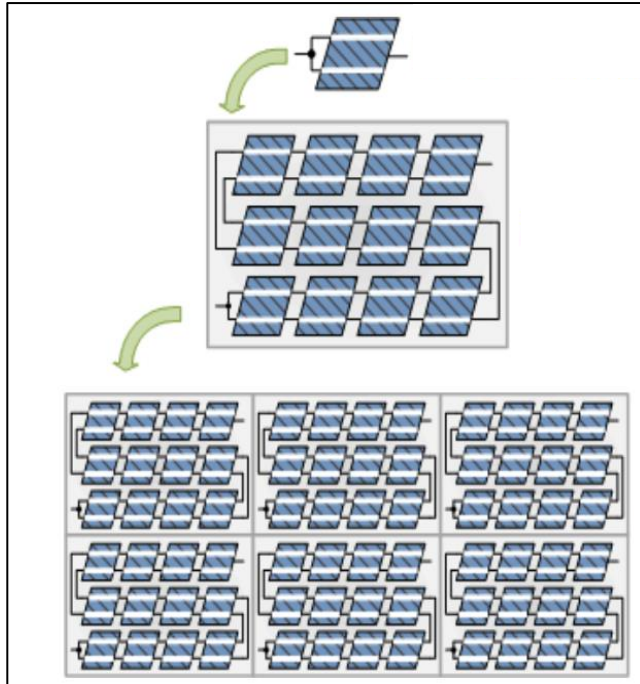

(a) PV cell → PV panel → PV array

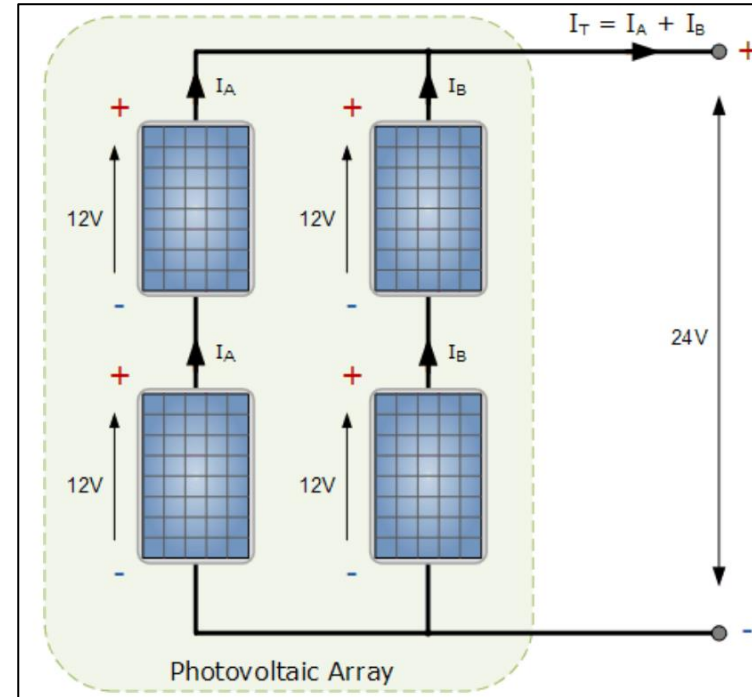

(b) Example of PV array

- Picture (a) shows PV Cell connection changes in to PV panel and connection of PV panel changes in to PV array.
- Picture (b) shows connection of PV panel. Two series circuit of PV panel is connected parallel. So the output voltage will be 24 V and total current equals to 7.5 A (assume that PV panel produces 3.75 A at full sun). Maximum power of PV array would be 180 W.


## ❖ Boost Converter

### ■ Definition

- Boost Converter is a switched-mode converter that is capable of producing an output voltage greater in magnitude than the input voltage (Step-up Converter)
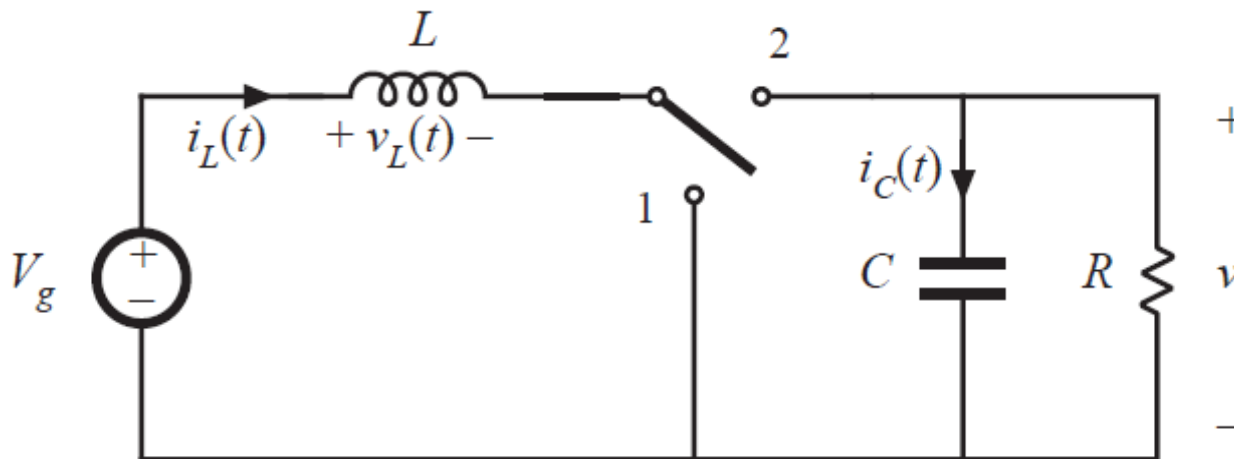
### ■ Description

- Switching position  $1 \rightarrow 2 \rightarrow 1$  occurs during one cycle
- Duty ratio(D) is the ratio of time when the switch is in position 1.
- D modulation range is between 0 and 1





## ❖ Boost Converter


- During one cycle, the equation below is obtained

$$\underbrace{(V_g)DT_s}_{\text{position 1}} + \underbrace{(V_g - V)(1 - D)T_s}_{\text{position 2}} = 0$$


- Output voltage is then

$$V_o = \frac{V_g}{1 - D}$$

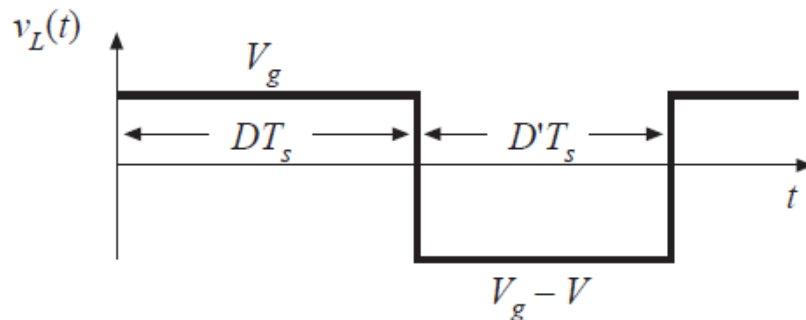- As seen from the voltage conversion ratio( $M(D)$ ), larger the duty ratio, larger the output voltage



<Switching cycle>

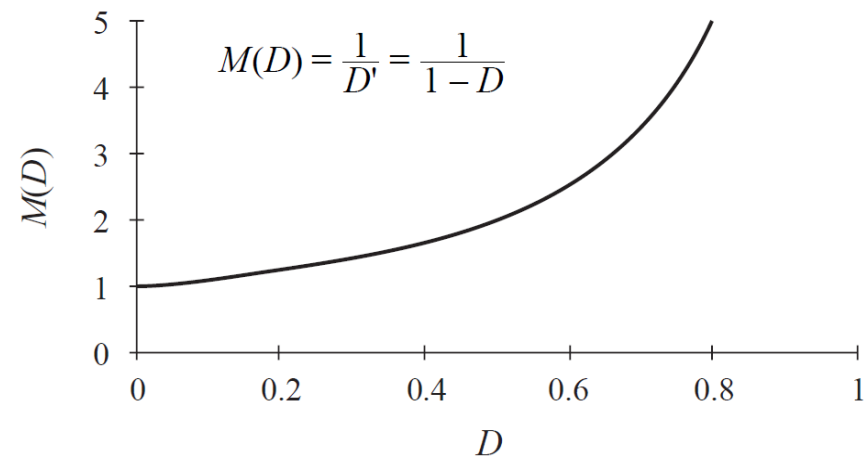

<Voltage conversion ratio>

## ❖ Determination of $\Delta i_L$ and $\Delta v_C$

### ■ Inductor Current Ripple

- Inductor current slope during subinterval 1:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g}{L}$$


- Inductor current slope during subinterval 2:

$$\frac{di_L(t)}{dt} = \frac{v_L(t)}{L} = \frac{V_g - V_o}{L}$$

$$2\Delta i_L (\text{Change in inductor current}) = \frac{V_g}{L} DT_s$$

- Solve for peak ripple:

$$\Delta i_L = \frac{V_g}{2L} DT_s$$

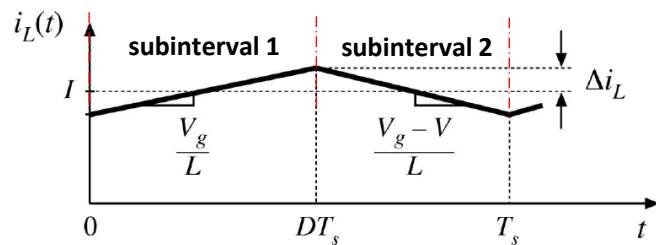

### ■ Capacitor Voltage Ripple

- Capacitor voltage slope during subinterval 1:

$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{-V_o}{RC}$$


- Capacitor voltage slope during subinterval 2:

$$\frac{dv_c(t)}{dt} = \frac{i_c(t)}{C} = \frac{I}{C} - \frac{V_o}{RC}$$

$$-2\Delta v_c (\text{Change in capacitor voltage}) = \frac{-V_o}{RC} DT_s$$



- Solve for peak ripple:

$$\Delta v_c = \frac{V_o}{2RC} DT_s$$

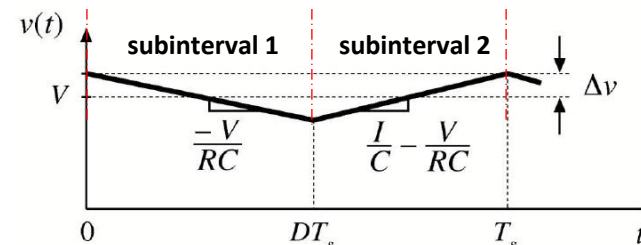
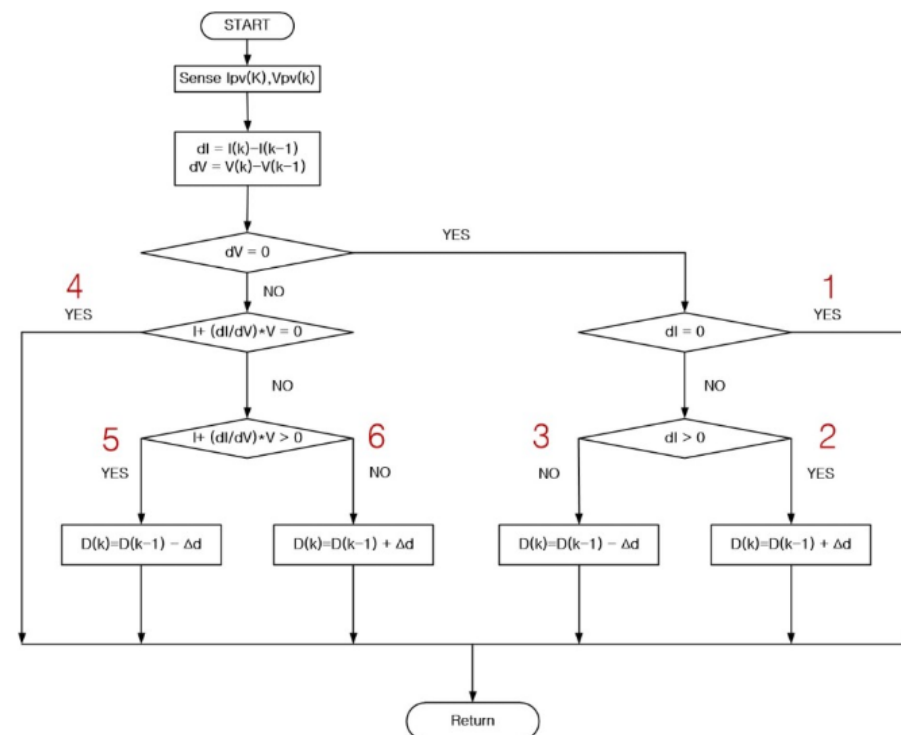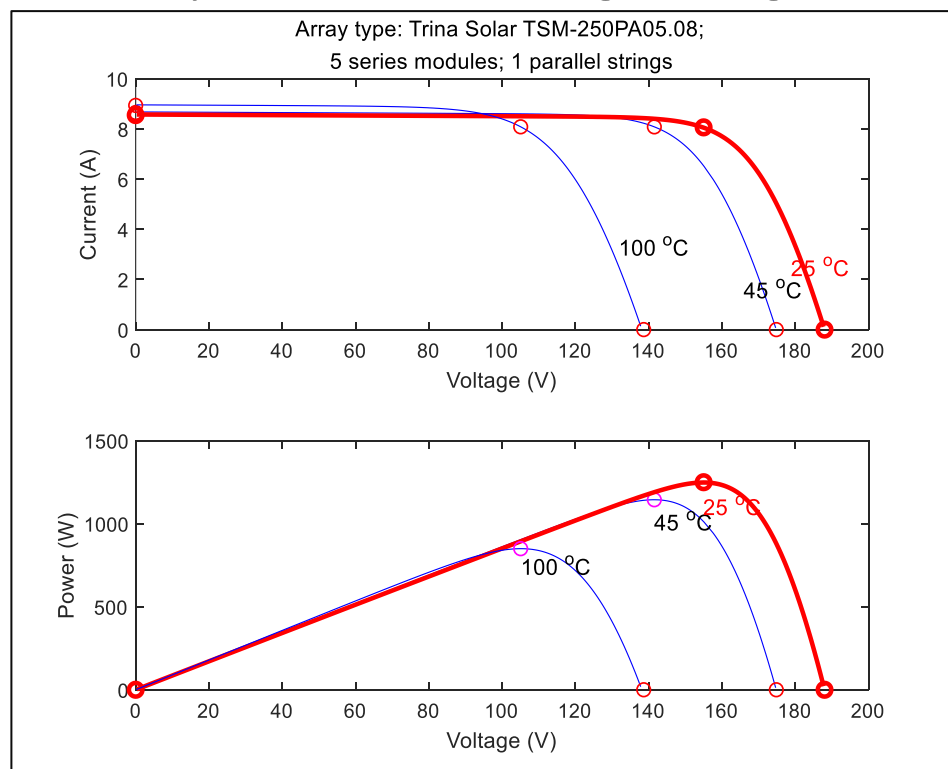
## ❖ What is MPPT



- System to maximize the output in any condition
- There are techniques to find the maximum power point (Perturb and Observe, **Incremental Conductance**, Constant Voltage, Current Sweep)
- Incremental Conductance algorithm predicts the effect of voltage change with PV array current and voltage changes.



# PV Generator Simulation


## PV Cell & Array

## ❖ PV Cell Circuit

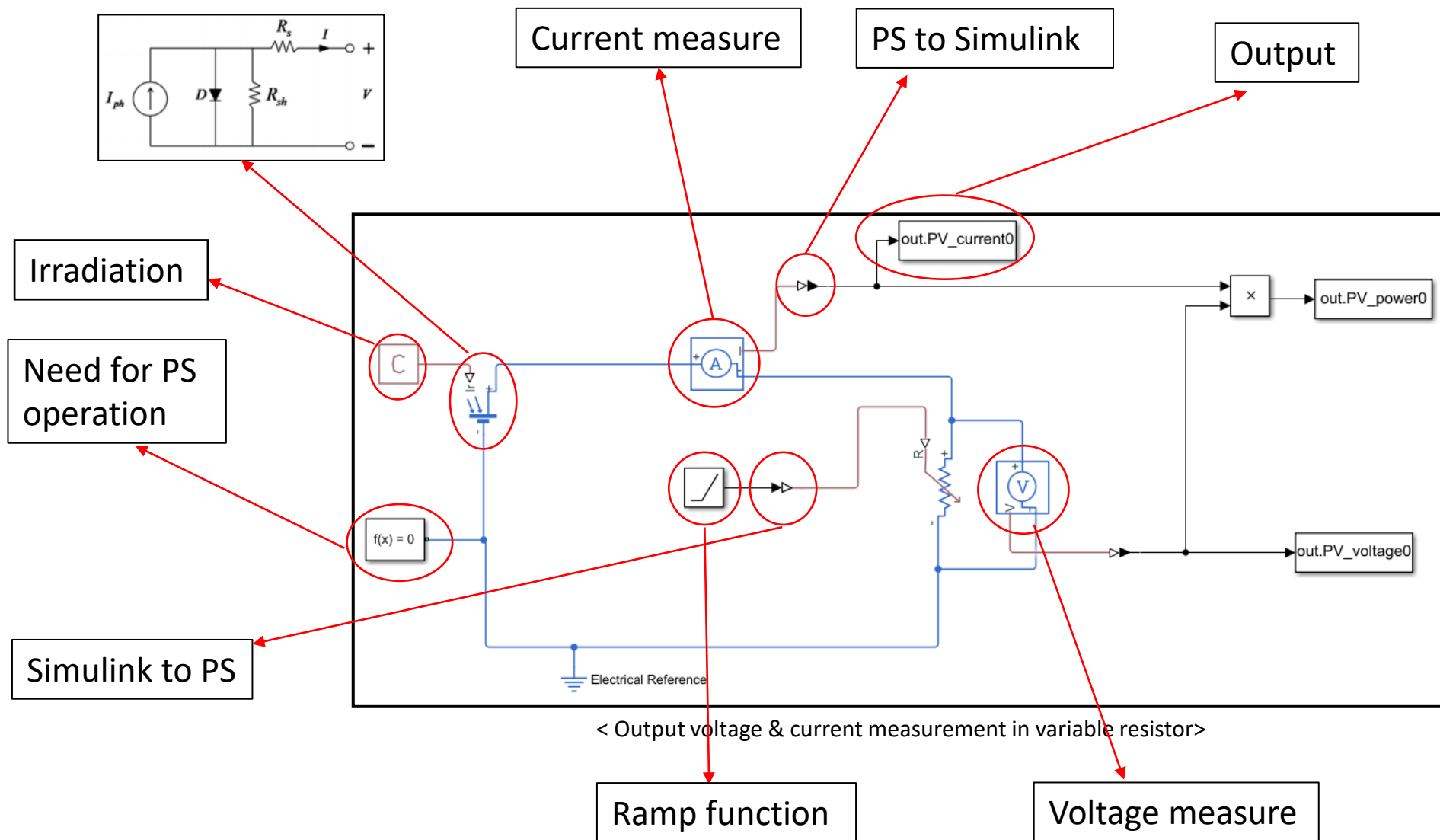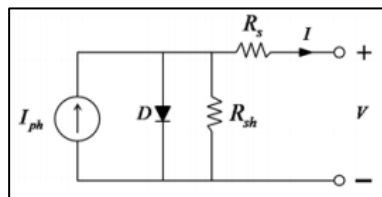

## ❖ PV Cell Circuit

out.PV\_current0

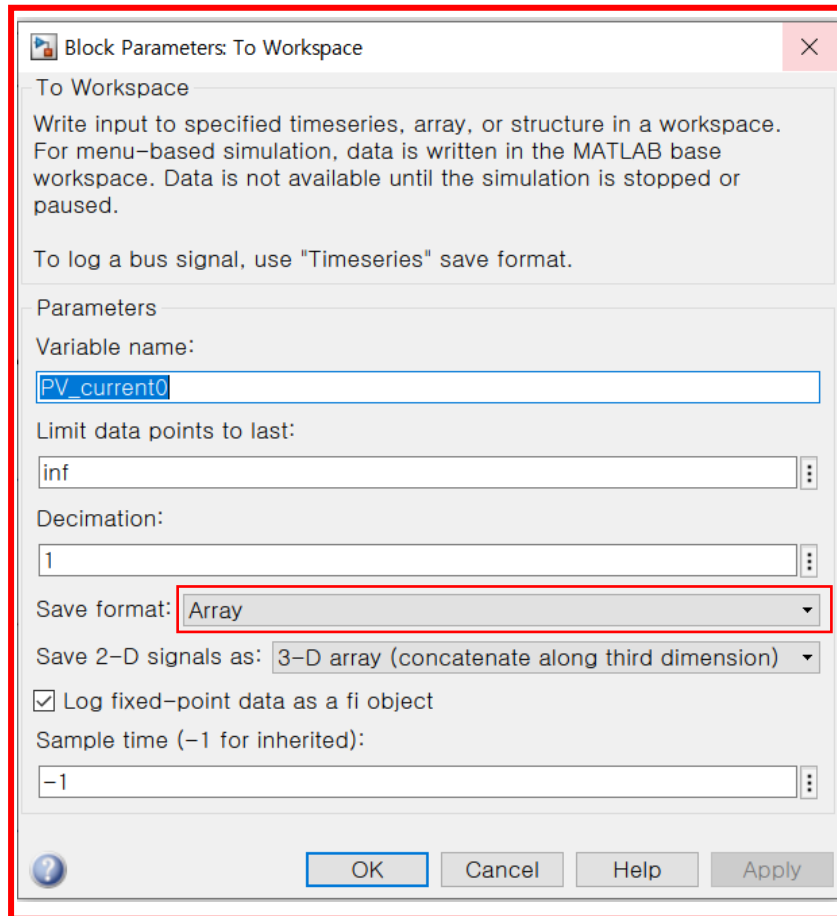


```
figure(1)
plot(out.PV_voltage0,out.PV_power0)
xlabel('PV Voltage(V)')
ylabel('PV Power(W)')
title('PV P-V Characteristic Curve')
|
figure(2)
plot(out.PV_voltage0,out.PV_current0)
xlabel('PV Voltage(V)')
ylabel('PV Current(A)')
title('PV I-V Characteristic Curve')
```


- This code must be written on the Matlab Workspace

## ❖ Simulation Result

P-V Curve

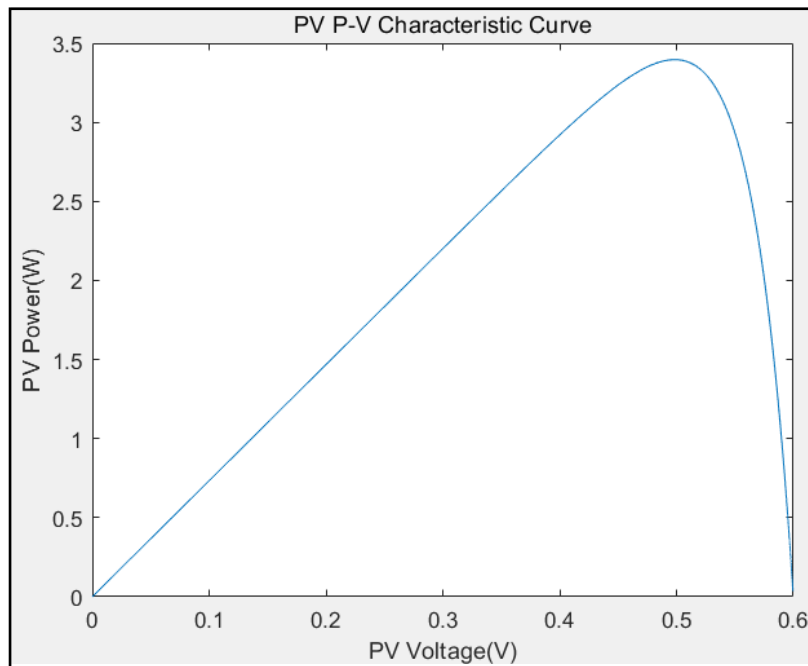


I-V Curve

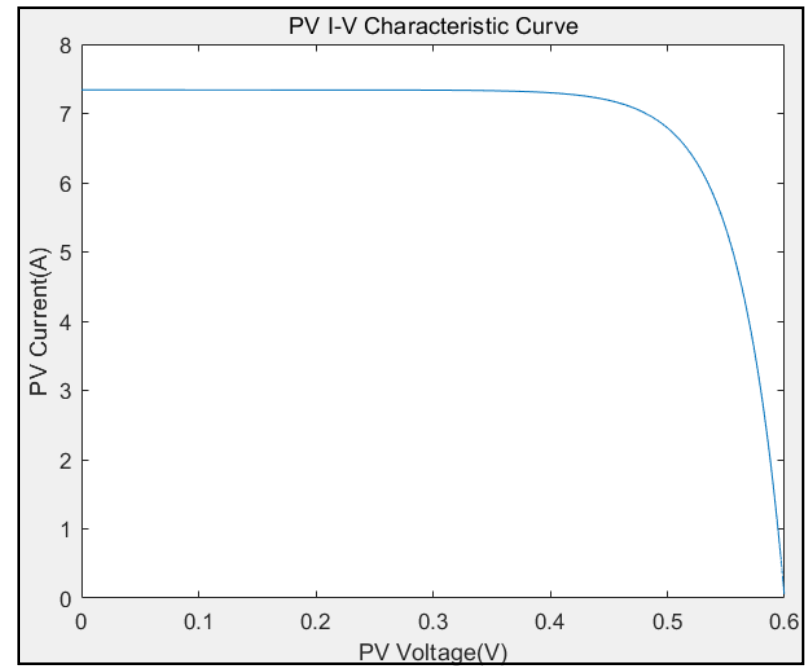

- Draw the plots of the P-V Curve & I-V Curve.

## ❖ PV Array Circuit

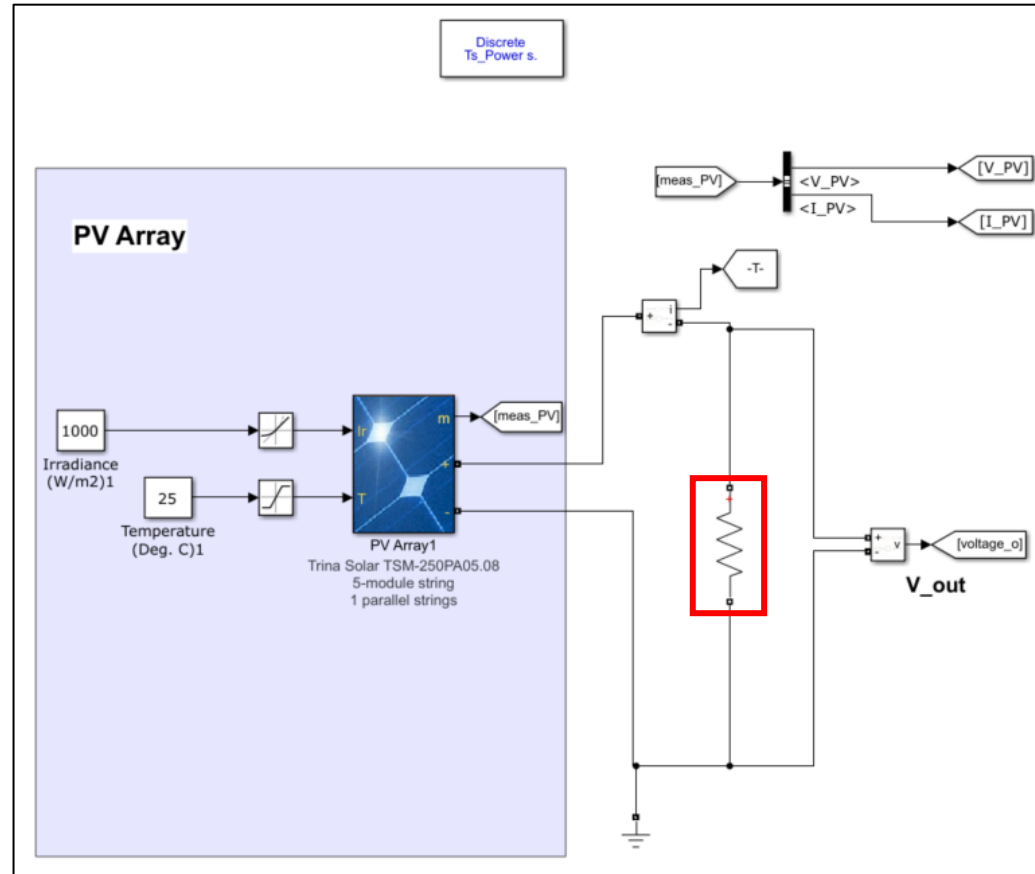

- Connect a parallel resistor to PV array.



## ❖ Maximum Power Operating Point

Block Parameters: PV Array

PV array (mask) (link)

Implements a PV array built of strings of PV modules connected in parallel. Each string consists of modules connected in series. Allows modeling of a variety of preset PV modules available from NREL System Advisor Model (Jan. 2014) as well as user-defined PV module.

Input 1 = Sun Irradiance, in W/m2, and Input 2 = Cell temperature, in deg.C.

Parameters Advanced

Array data

Parallel strings 1

Series-connected modules per string 5

Module data

Module: Trina Solar TSM-250PA05.08

Maximum Power (W) 249.86 Cells per module (Ncell) 60

Open circuit voltage Voc (V) 37.6 Short-circuit current Isc (A) 8.55

Voltage at maximum power point Vmp (V) 31 Current at maximum power point Imp (A) 8.06

Temperature coefficient of Voc (%/deg.C) -0.35 Temperature coefficient of Isc (%/deg.C) 0.06

Display I-V and P-V characteristics of ...

array @ 1000 W/m2 & specified temperatures

T\_cell (deg. C) [ 45 25 100 ]

Plot

Model parameters

Light-generated current IL (A) 8.5795

Diode saturation current I0 (A) 2.0381e-10

Diode ideality factor 0.99766


Shunt resistance Rsh (ohms) 301.8149

Series resistance Rs (ohms) 0.247

OK Cancel Help Apply

- Check I-V & P-V Curve of PV array.
- Changing module data and the array data yields waveforms of different voltage ranges.
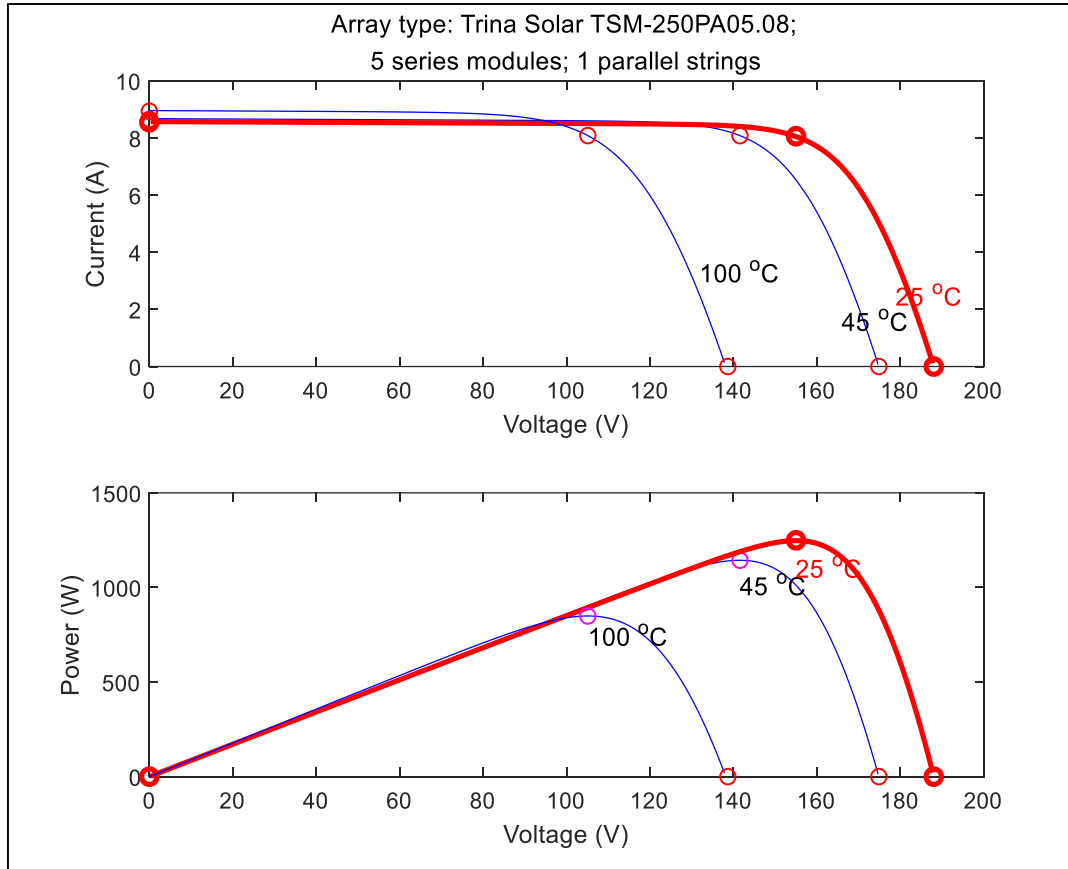
## ❖ Maximum Power Operating Point (MPOP)



- Derive basic PV generating power at 1000W/m<sup>2</sup> and 25 deg.
- This plot implies a MPOP and voltage operation range.

- Change the resistance, check the output voltage and current and draw the PV V-I curve.

(Temperature = 25°C)

Resistance ( $\Omega$ )	Voltage (V)	Current (A)

- Change the resistance, figure out the MPOP.  
(Temperature = 25°C)


Resistance ( $\Omega$ )	Voltage (V)	Current (A)

# PV Generator Simulation

## Boost Converter



## ❖ Boost Converter Circuit

Boost Converter

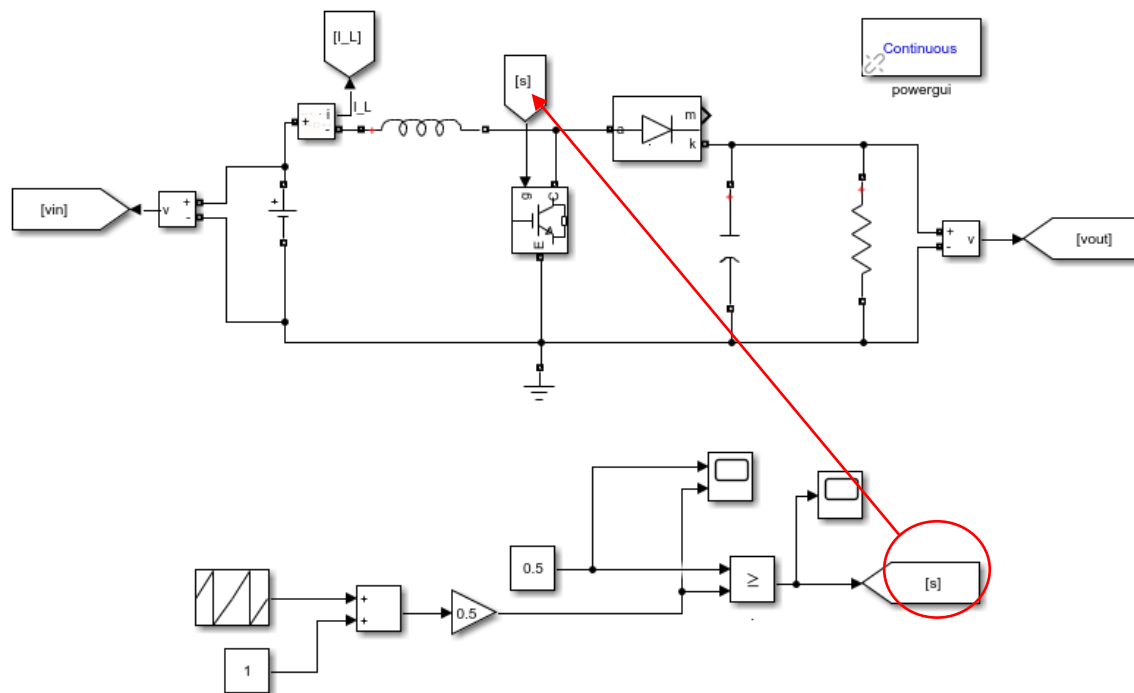

- When the Boost Converter is connected to the ideal voltage source, the output voltage can be boosted according to the duty ratio ( $D$ ).
- Figure out the duty ratio in the right side.  $D=??$

## ❖ Switching signal

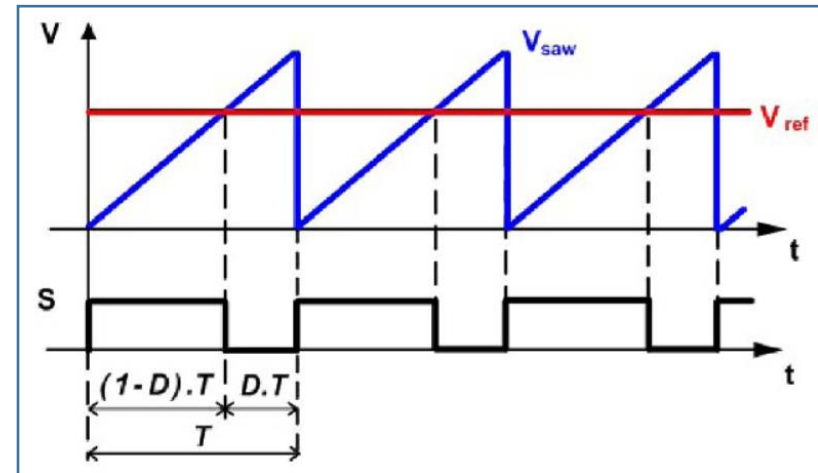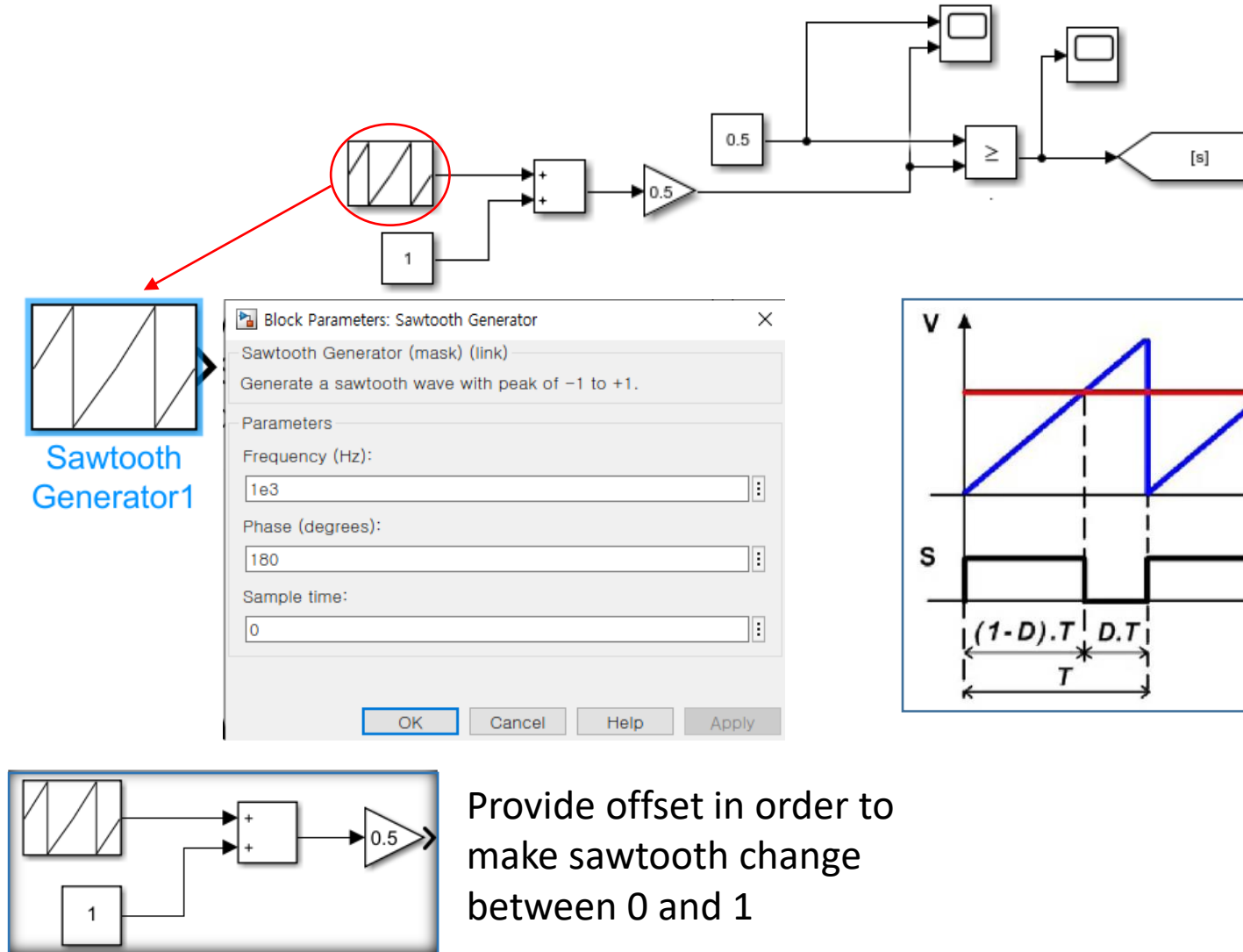

## ❖ Specification of System Circuit Component (Boost Converter)

Parameter	Given Value
Input Voltage	100 V
On/Off Switch	IGBT/Diode
Capacitance (C)	5000 $\mu$ F
Inductance (L)	80 mH
Resistance (R)	5 $\Omega$



## ❖ Simulation Result


$$D = 0.5$$

$$V_{out} = 2 \times V_{in}$$

Output Voltage

Input Voltage

Inductor current

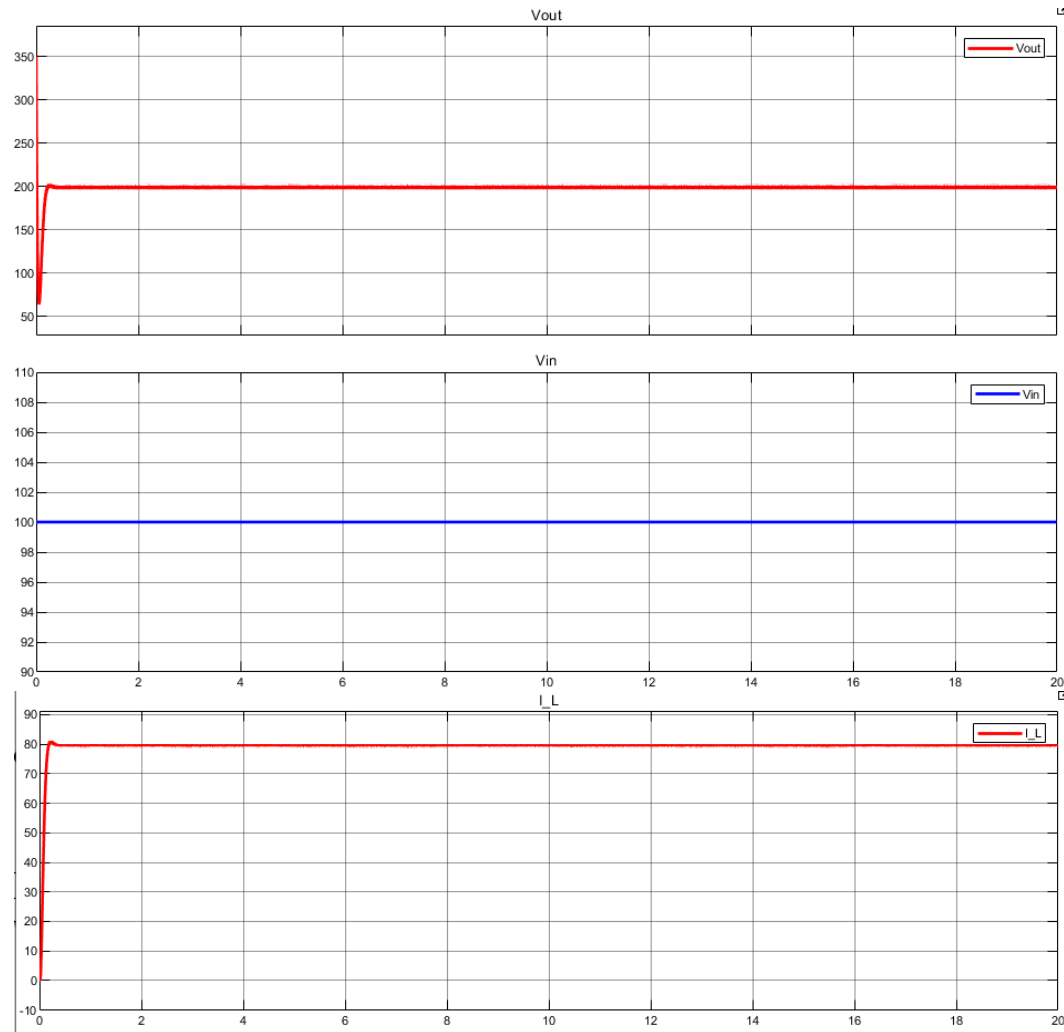

- Plot the output voltage ripple & inductor current and figure out the magnitude of ripple with changing the capacitance

Capacitance (C)	Voltage Ripple	Current Ripple


- Plot the output voltage ripple & inductor current and figure out the magnitude of ripple with changing the inductance

Inductance (L)	Voltage Ripple	Current Ripple

# PV Generator Simulation

## PV Array & Boost Converter Design

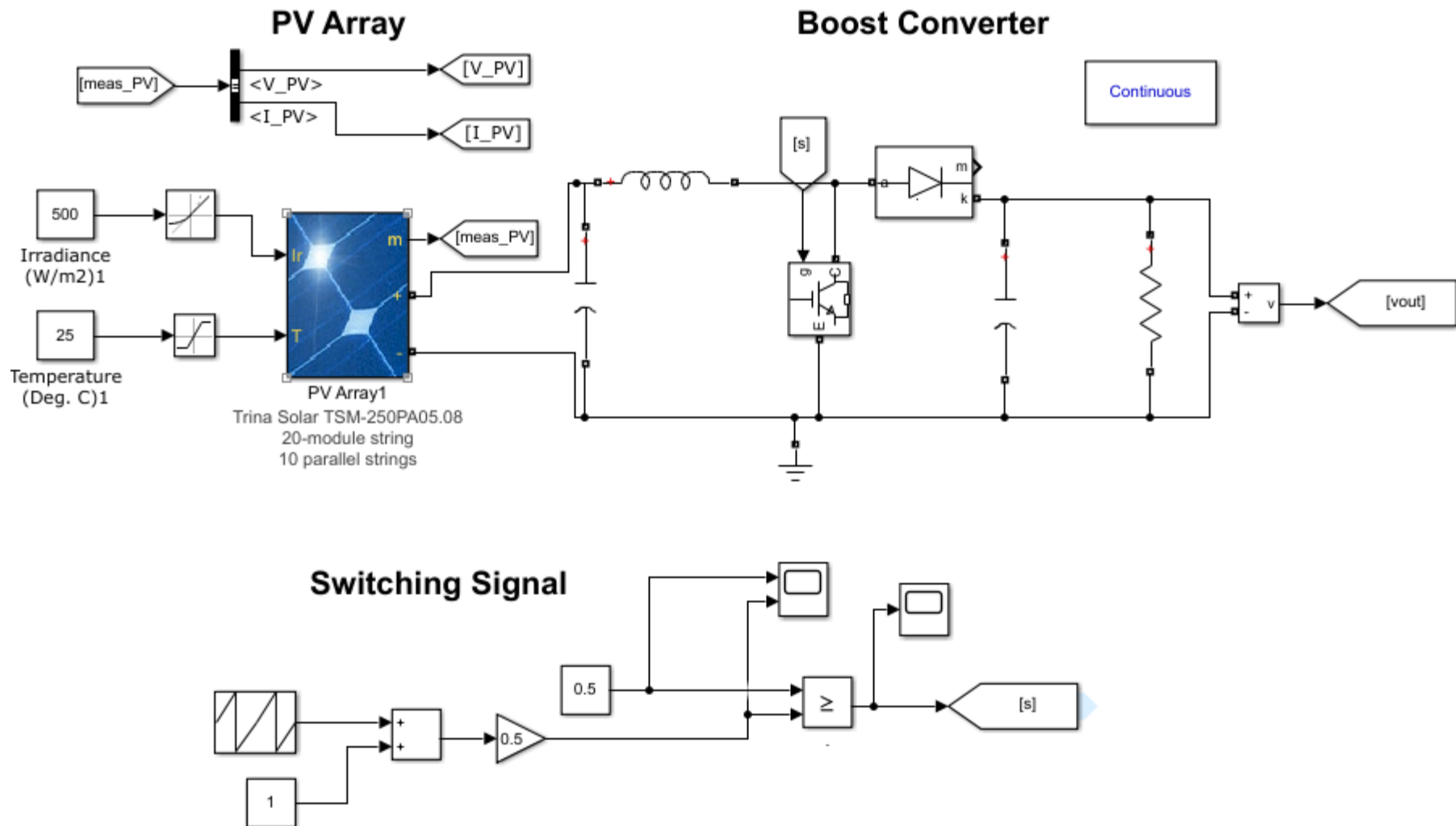
## ❖ PV Array and Boost Converter System Circuit



## ❖ Specification of System Circuit Components (PV Array & Boost Converter)

Parameter	Given Value
Irradiance	500 W/m <sup>2</sup>
Temperature	25 Deg.
PV Module data	Trina Solar TSM-250PA05.08
PV Parallel strings	10 parallel strings
PV Series connected modules per string	20 module string
PV side Capacitance (C)	1000 $\mu$ F
Output side Capacitance (C)	5000 $\mu$ F
Inductance (L)	80 mH

## ❖ Simulation Result

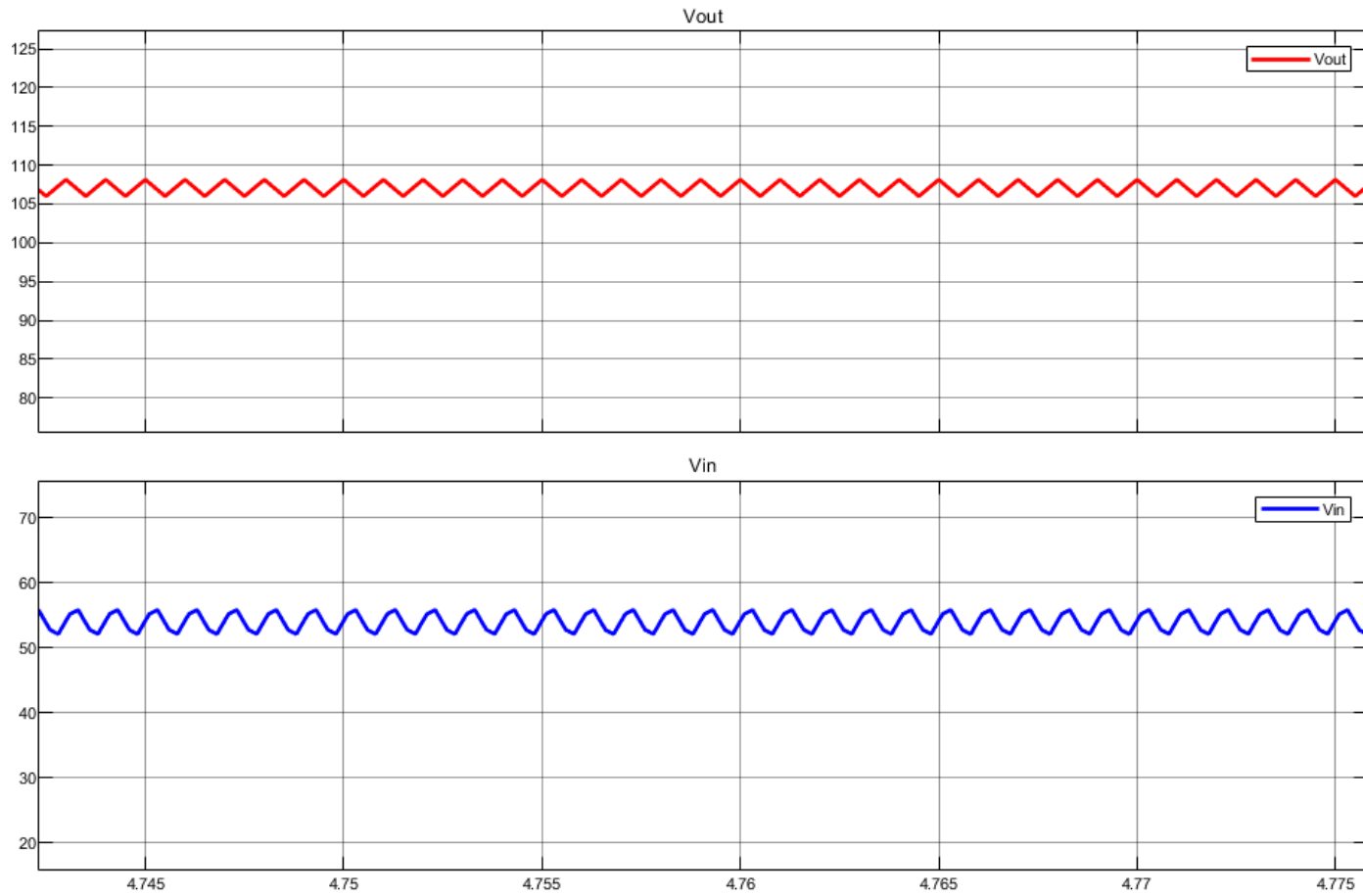

- Output voltage is doubled. Why?


- Change duty ratio (D) of Boost converter and check the output voltage variation.

Duty Ratio (D)	Input voltage (V)	Output voltage (V)


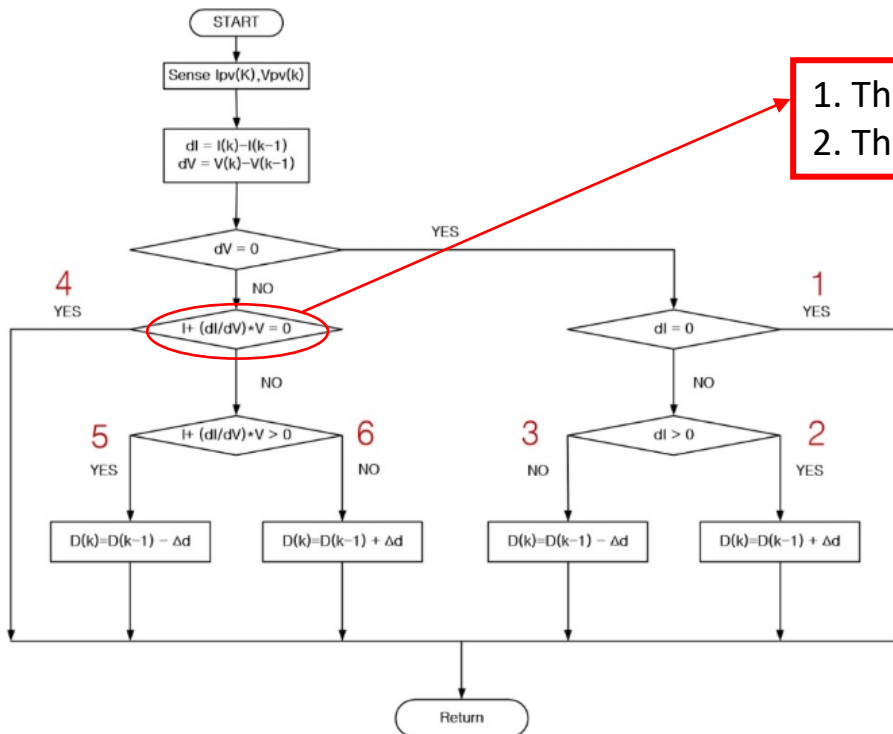
## ❖ Using MPPT Controller

- Incremental Conductance Technique to find the maximum power point




1. Think about the equation  $P = VI$
2. Think about the P-V curve

Matlab  
Function  
Block



# Boost Converter connected PV Array


## ❖ PV+Boost+MPPT Controller circuit

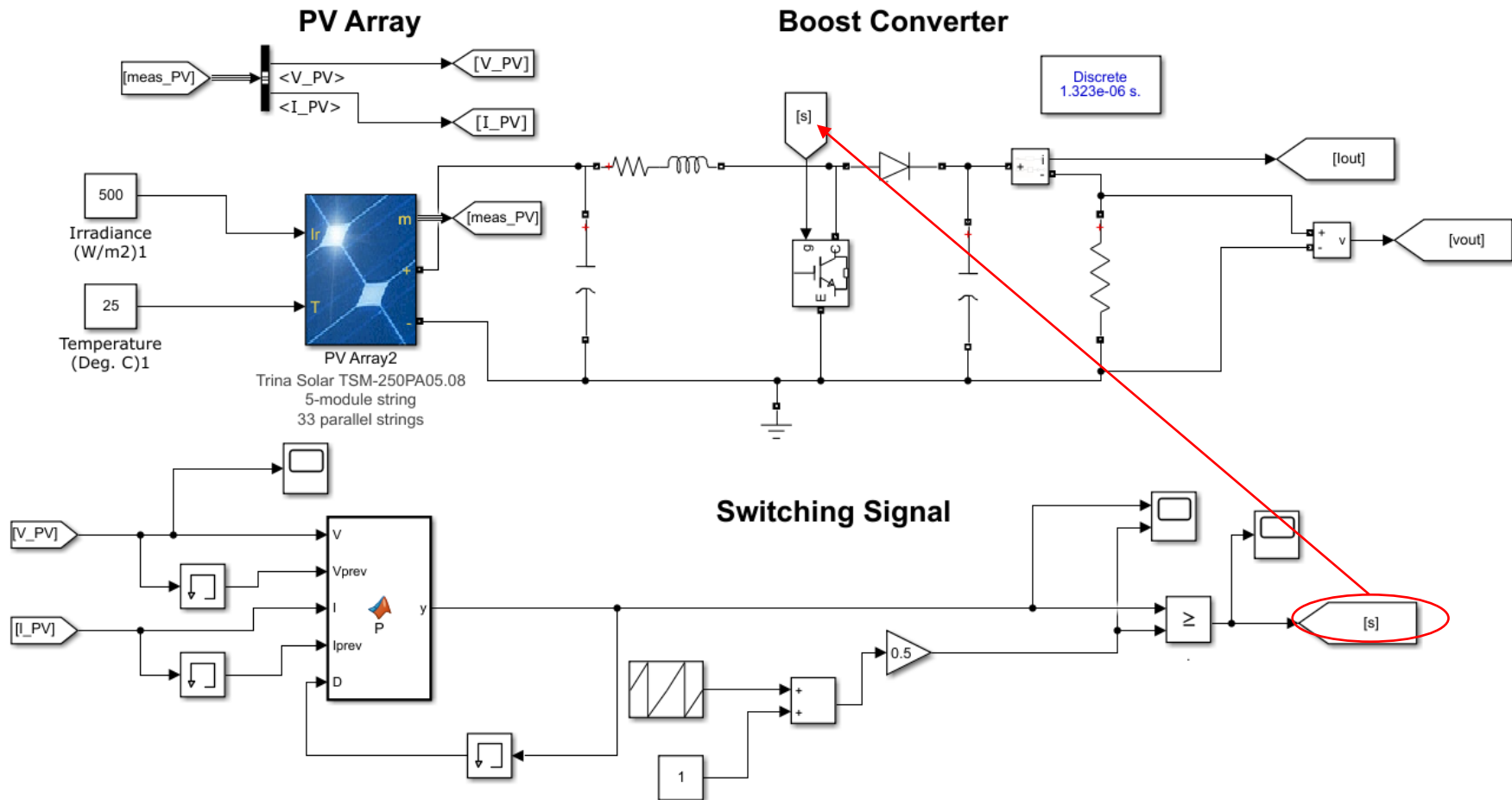

$Ts\_Power = 1.322751322751323e-06$  ;  
 $Ts\_Control = 2.645502645502646e-05$  ;

Time step (write in matlab)


## ❖ MPPT Controller

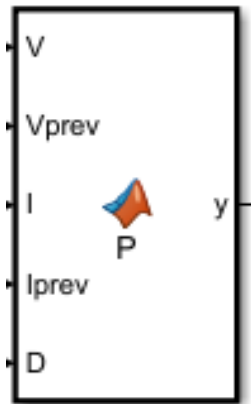

- ① Right click
- ② explore



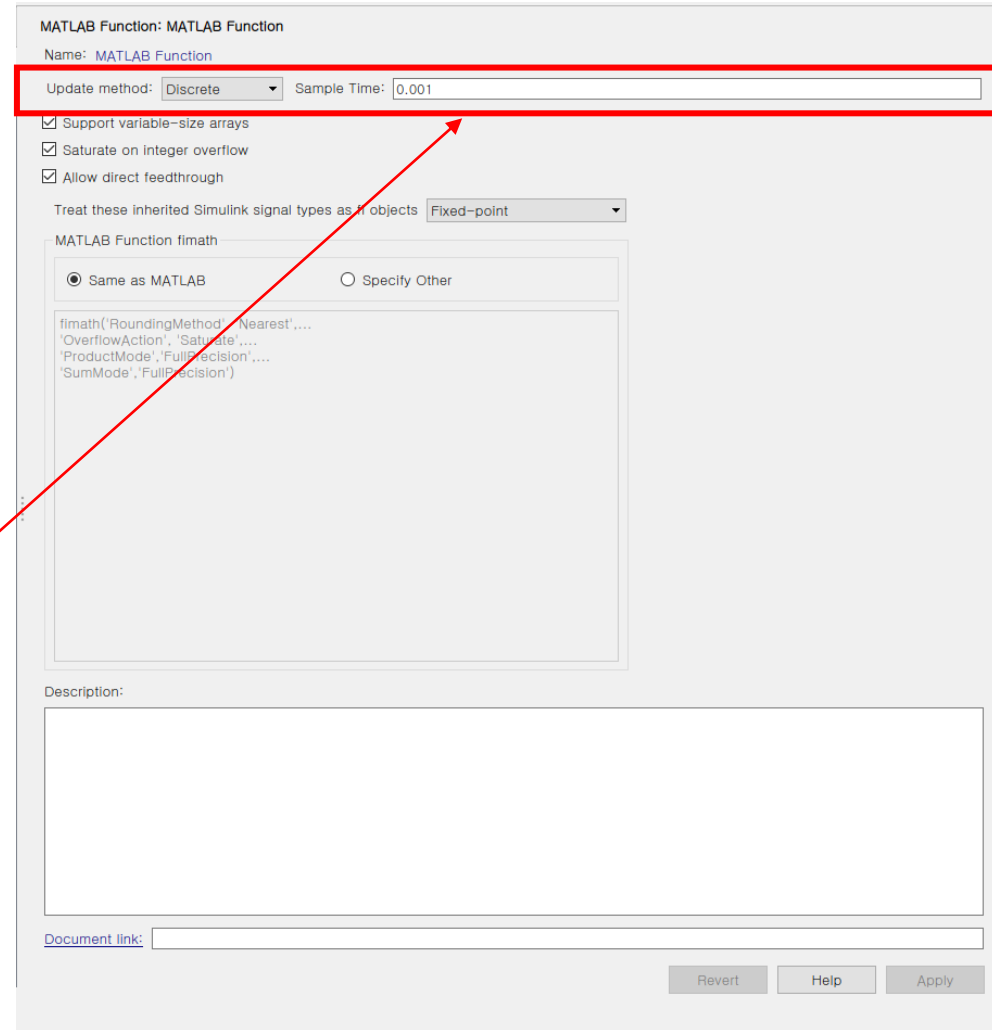Sample Time should be same as switching frequency!



 
# Discussion (Boost Converter + PV)

- Write the code  
(Check the algorithm p.33)



```
function y = P(V, Vprev, I, Iprev,D)
```



```
end
```

- Plot the duty ratio and input/output voltage of the converter
- Check the output power of the PV array and compare with the output power of the converter.

